

# Analysis of Inductive WPT



Jan Kracek, Milos Mazanek

Czech Technical University in Prague



# Outline

- » Introduction
- » Efficiency
- » Power balance
- » Input impedance
- » Conclusion




# Outline


- » Introduction
- » Efficiency
- » Power balance
- » Input impedance
- » Conclusion




# Introduction

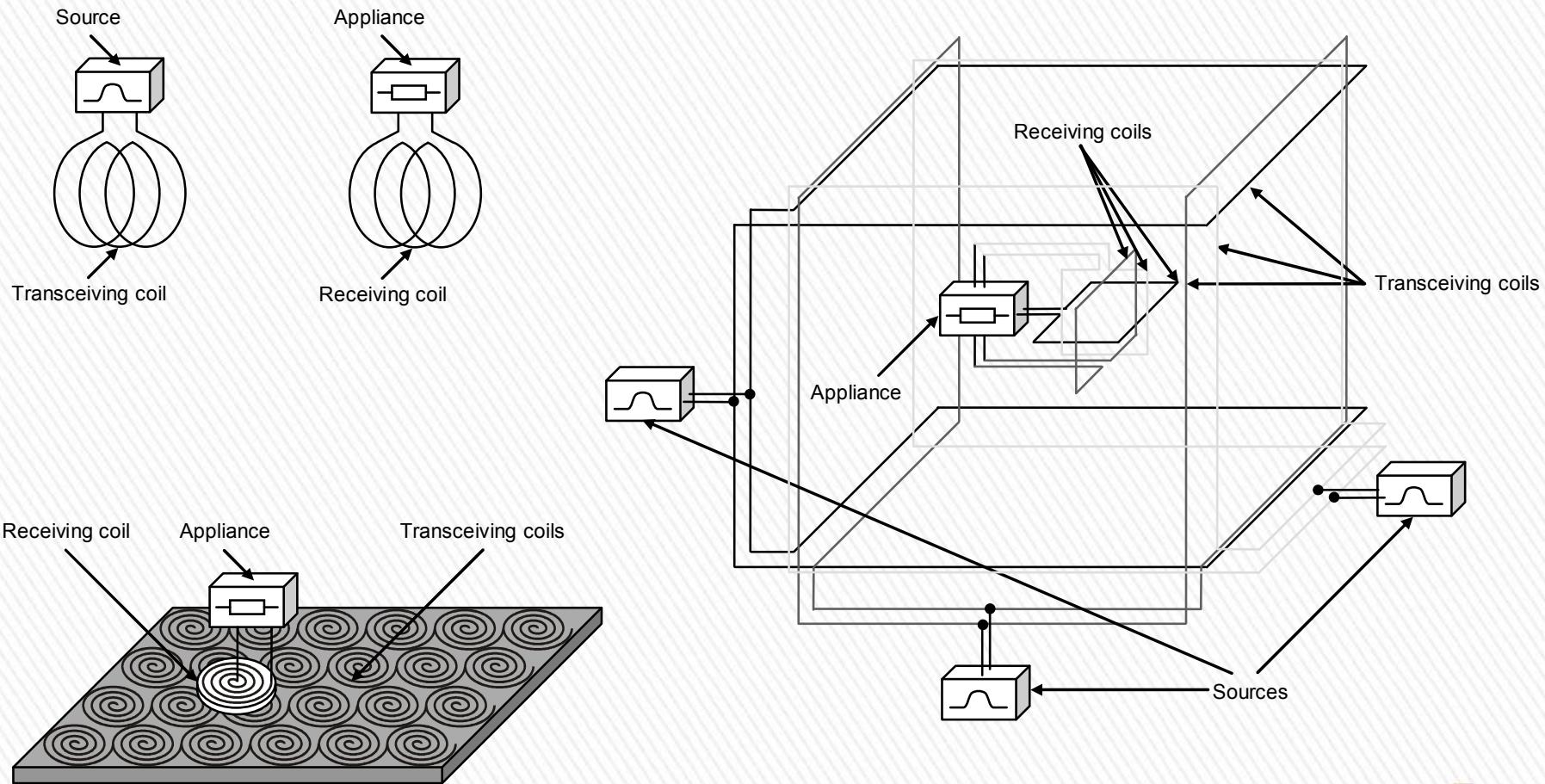


# General WPT Chain

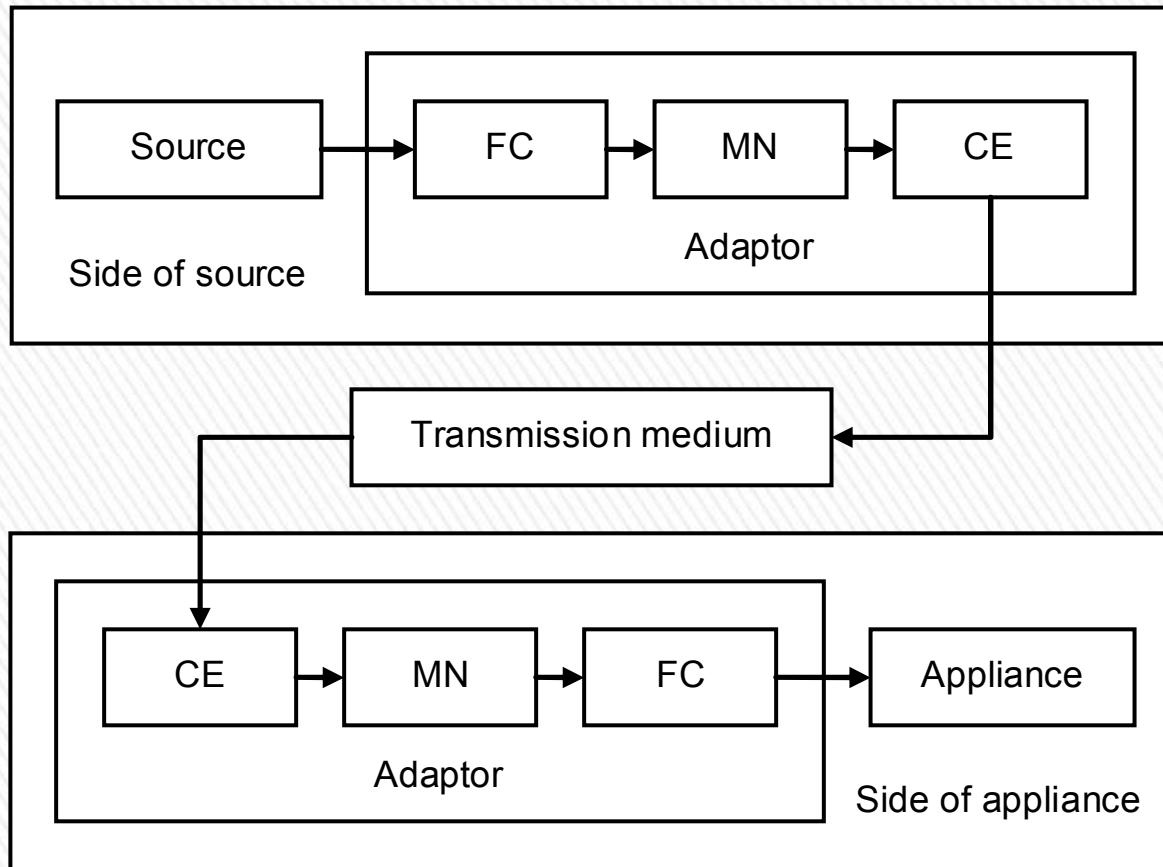

# Circuit Model

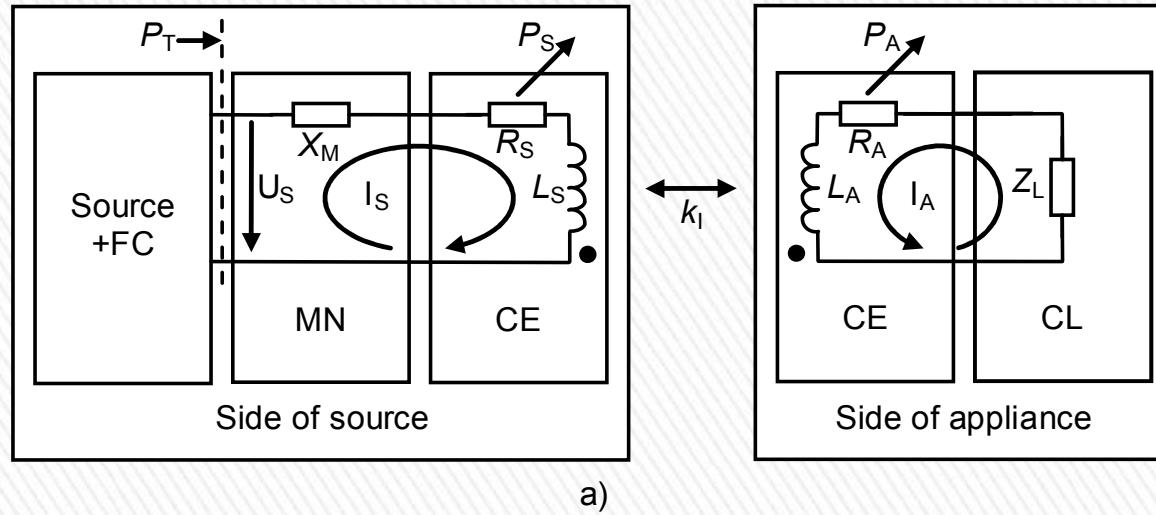

a)

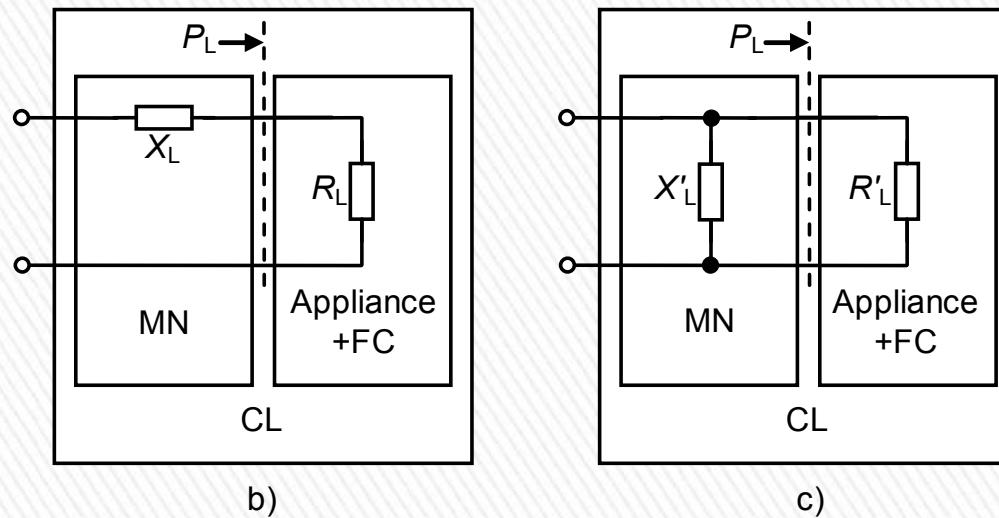

b)

c)




# Outline

- » Introduction
- » Efficiency
- » Power balance
- » Input impedance
- » Conclusion

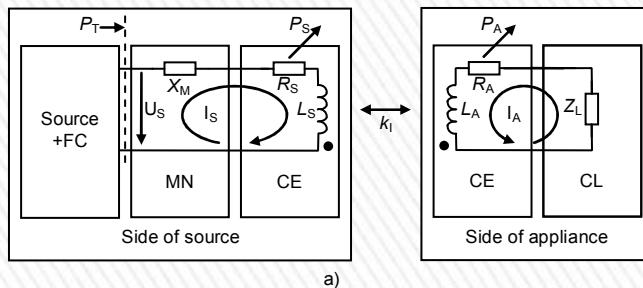
# Efficiency Definition

- » Main losses are caused by resistances of transceiving and receiving coils.

$$\» \eta_I = \frac{P_L}{P_T} = \frac{P_L}{P_A + P_L + P_S}$$



a)

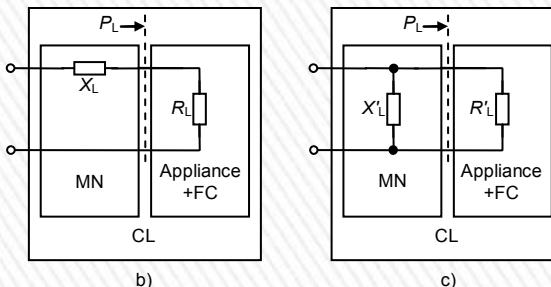

b)

c)



# Efficiency Derivation (1)

$$\gg \eta_I = \frac{R_L X_K^2}{\left( (R_A + R_L)^2 + (X_A + X_L)^2 \right) R_S + (R_A + R_L) X_K^2}$$

$$X_A = \omega L_A, \quad X_S = \omega L_S, \quad X_K = \omega k_I \sqrt{L_A L_S}$$

$$\frac{X_K}{\sqrt{X_A X_S}} = k_I, \quad \frac{X_A}{R_A} = Q_A, \quad \frac{X_L}{R_A} = -Q'_A, \quad \frac{X_A}{R_L} = Q_L, \quad \frac{X_S}{R_S} = Q_S$$

$$\gg \eta_I = \frac{k_I^2 Q_A Q_S \frac{Q_A}{Q_L}}{\left( 1 + \frac{Q_A}{Q_L} \right)^2 + (Q_A - Q'_A)^2 + k_I^2 Q_A Q_S \left( 1 + \frac{Q_A}{Q_L} \right)}$$

# Efficiency Derivation (2)

$$\gg \kappa = k_I \sqrt{Q_A Q_S}, \rho = \frac{Q_A}{Q_L}, \xi = Q_A - Q'_A$$

$$\eta_I = \frac{\kappa^2 \rho}{(1 + \rho)^2 + \xi^2 + \kappa^2 (1 + \rho)}$$

$\gg R, L, C, \omega, (X) \rightarrow k_I, Q_A, Q'_A, Q_L, Q_S \rightarrow \kappa, \rho, \xi \rightarrow$   
 $\max(\eta_I(\rho, \xi)) \rightarrow \rho = \sqrt{1 + \kappa^2}, \xi = 0 \rightarrow$   
 $\kappa, \rho, \xi \rightarrow k_I, Q_A, Q'_A, Q_L, Q_S \rightarrow R, L, C, \omega, (X)$




# Maximal Efficiency, Optimal Conditions

$$\gg R_L = \sqrt{R_A^2 + \omega^2 k_I^2 L_A L_S} \frac{R_A}{R_S}$$

$$X_L = -\omega L_A$$


$$\gg \eta_I = \frac{(k_I Q)^2}{\left(1 + \sqrt{1 + (k_I Q)^2}\right)^2}$$

$$Q = \sqrt{Q_A Q_S}$$

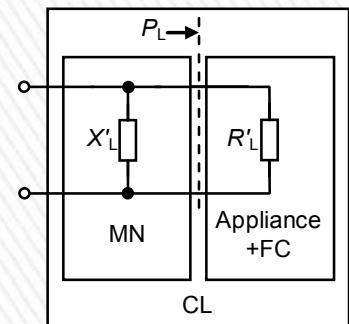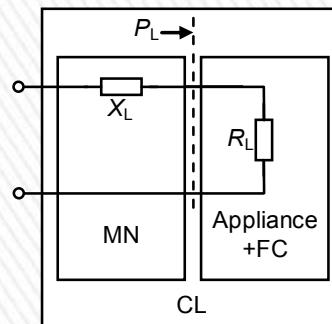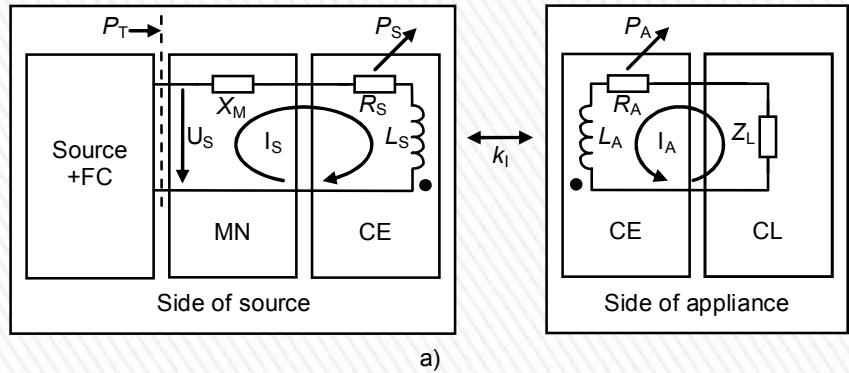
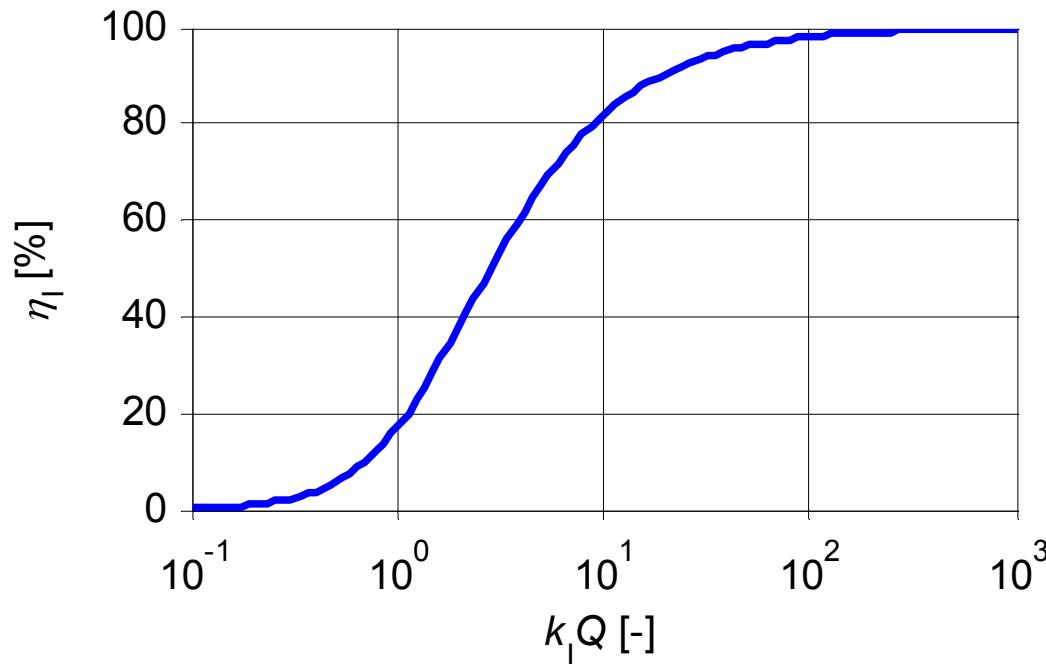
# Maximal Efficiency

$$\gg \eta_I = \frac{(k_I Q)^2}{\left(1 + \sqrt{1 + (k_I Q)^2}\right)^2}$$






# Max. eff., Opt. Con. – Dual Case

$$\gg R_L + jX_L = \frac{R'_L X'^2_L}{R'^2_L + X'^2_L} + j \frac{R'^2 L'_L X'_L}{R'^2 L'_L + X'^2 L'_L}$$

$$\gg R'_L = \frac{\omega^2 L_A^2}{\sqrt{R_A^2 + \omega^2 k_I^2 L_A L_S \frac{R_A}{R_S}}} + \sqrt{R_A^2 + \omega^2 k_I^2 L_A L_S \frac{R_A}{R_S}}$$
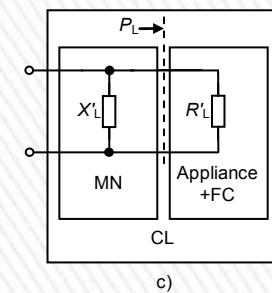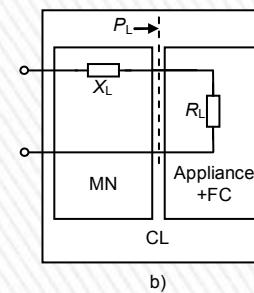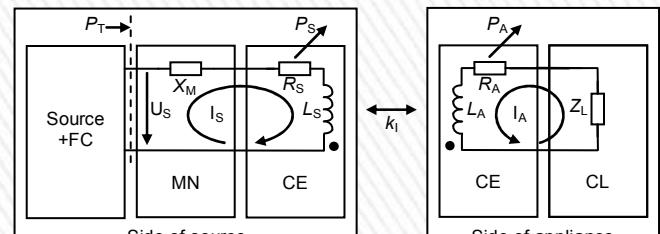
$$X'_L = -\omega L_A - \frac{R_A^2 + \omega^2 k_M^2 L_A L_S \frac{R_A}{R_S}}{\omega L_A}$$



# Outline


- » Introduction
- » Efficiency
- » Power balance
- » Input impedance
- » Conclusion



# Maximal Appliance Power, Optimal Condition

»  $\max(P_L(X_M))$

»  $X_M = -\omega L_S$

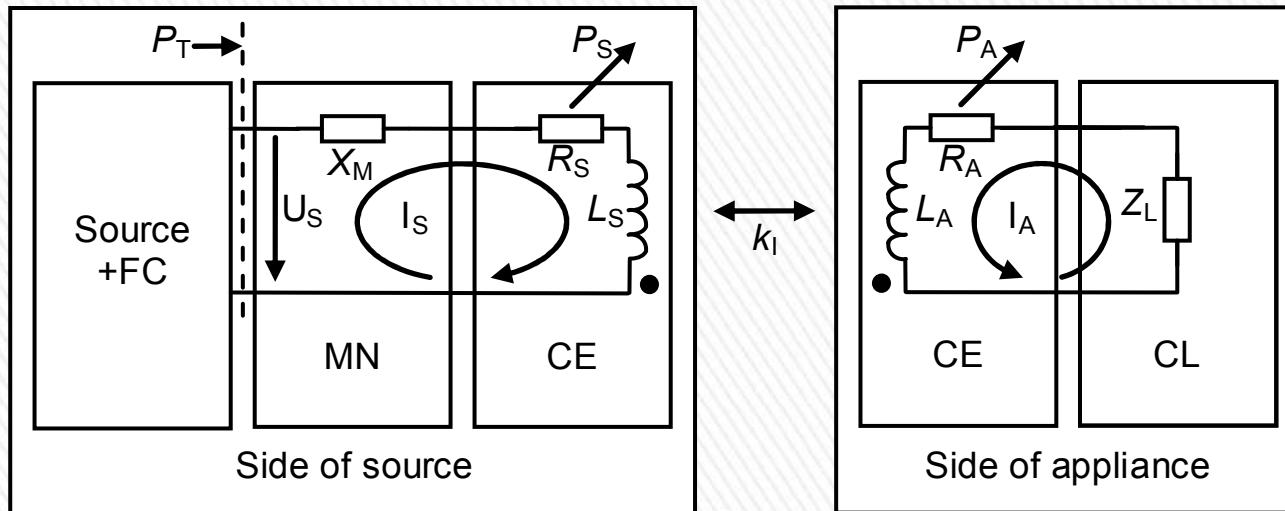


# Power Balance (1)


$$\gg R_L = \sqrt{R_A^2 + \omega^2 k_I^2 L_A L_S} \frac{R_A}{R_S}$$

$$\gg X_L = -\omega L_A$$


$$\gg X_M = -\omega L_S$$

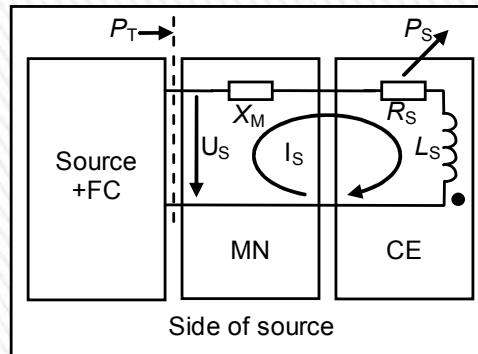

a)

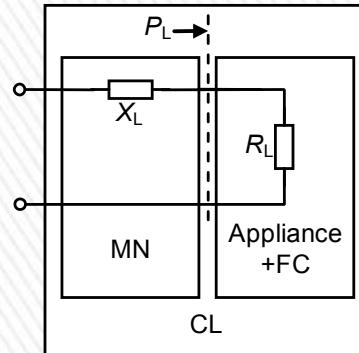

b)

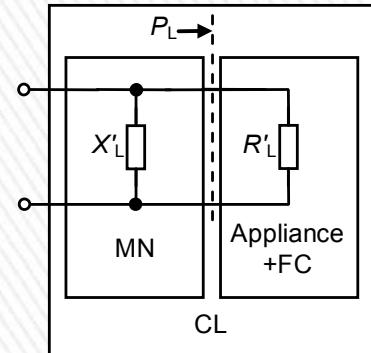

c)

# Power Balance (2)


$$\gg P_A = \frac{(k_I Q)^2}{\underbrace{\left(1 + (k_I Q)^2 + \sqrt{1 + (k_I Q)^2}\right)^2}_{p_A}} \frac{|U_s|^2}{R_s}$$

$$\gg P_L = \frac{(k_I Q)^2 \sqrt{1 + (k_I Q)^2}}{\underbrace{\left(1 + (k_I Q)^2 + \sqrt{1 + (k_I Q)^2}\right)^2}_{p_L}} \frac{|U_s|^2}{R_s}$$



$$\gg P_S = \frac{\left(1 + \sqrt{1 + (k_I Q)^2}\right)^2}{\underbrace{\left(1 + (k_I Q)^2 + \sqrt{1 + (k_I Q)^2}\right)^2}_{p_S}} \frac{|U_s|^2}{R_s}$$



# Power Balance (3)

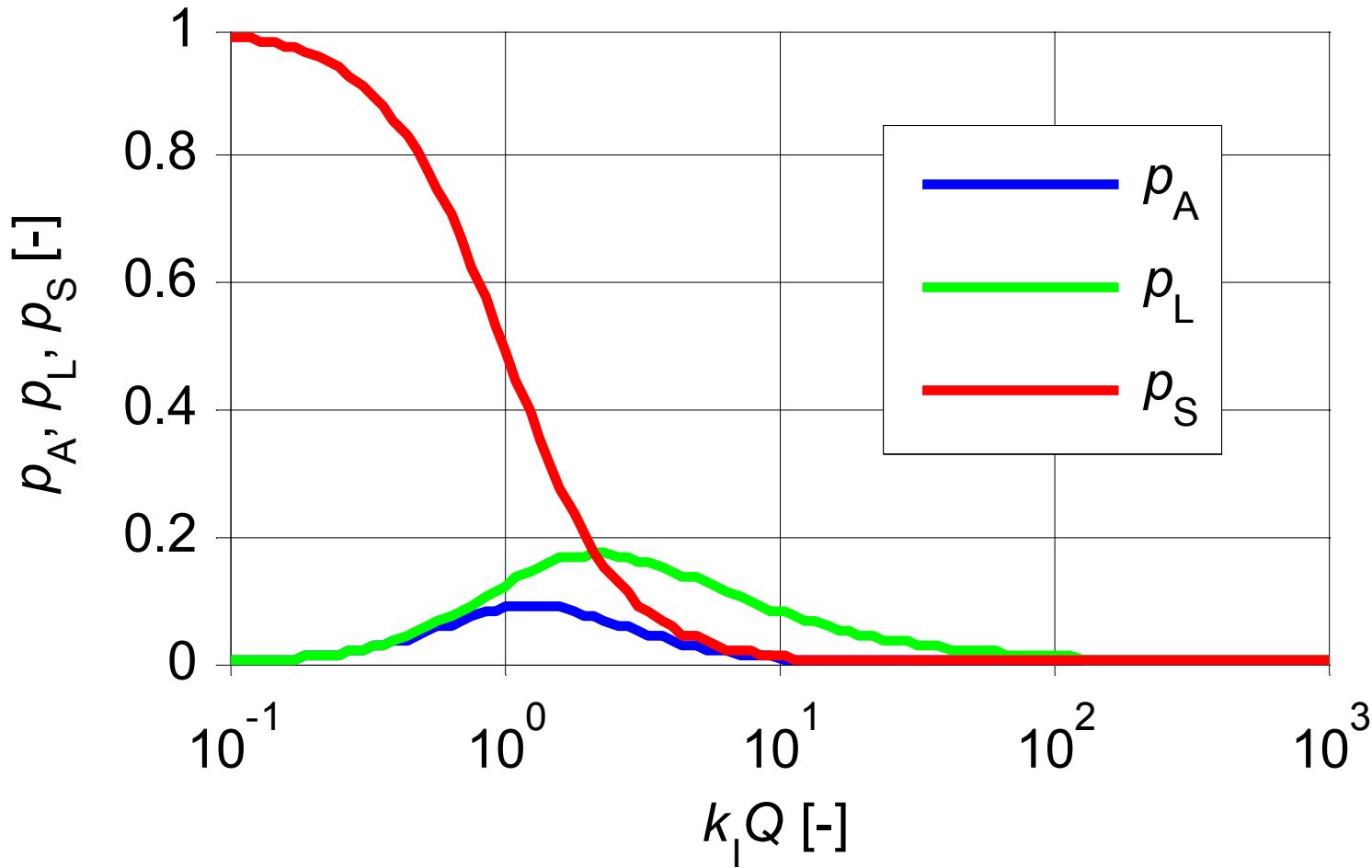

# Efficiency and Power Balance

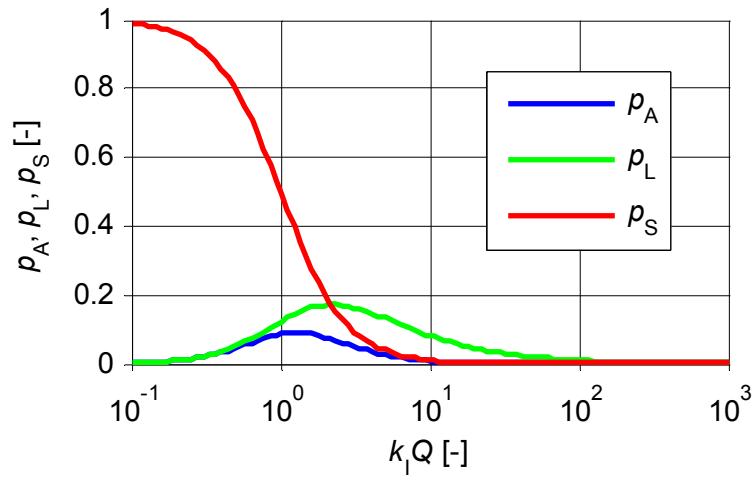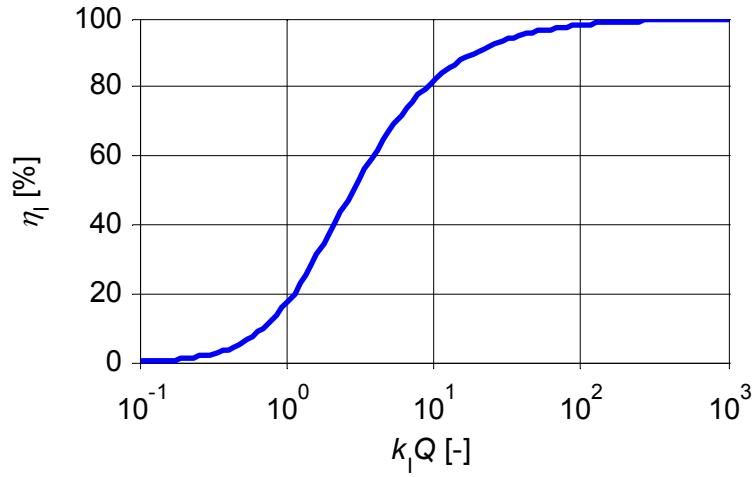


# Outline

- » Introduction
- » Efficiency
- » Power balance
- » Input impedance
- » Conclusion



# Input Impedance (1)

$$\gg Z_S = \frac{U_S}{I_S}$$

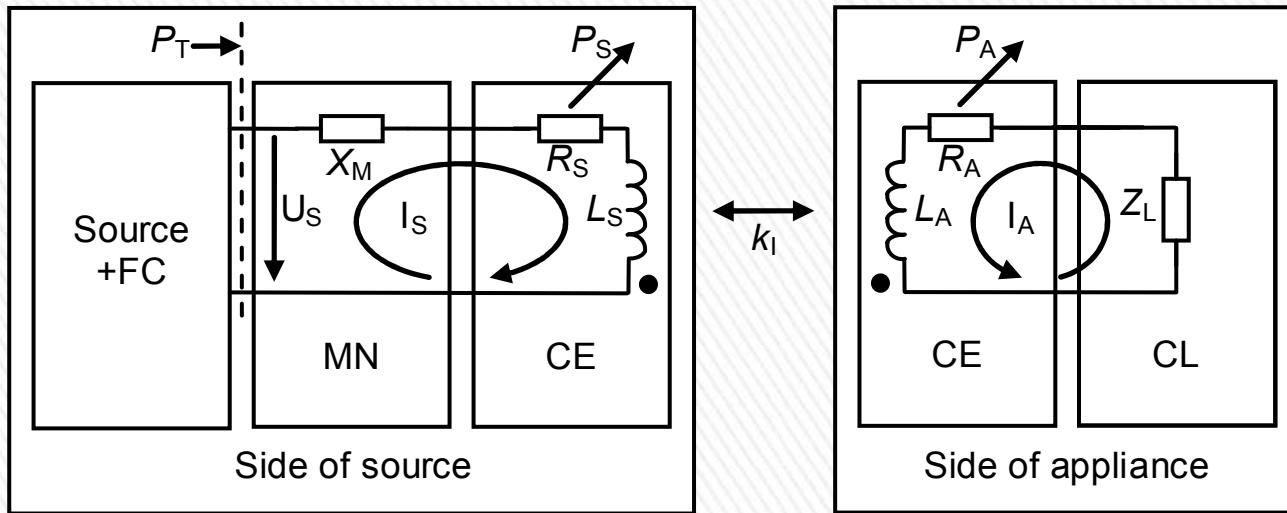

# Input Impedance (2)

$$\gg Z_s = \frac{U_s}{I_s} = R_s + \frac{(R_A + R_L) X_K^2}{(R_A + R_L)^2 + (X_A + X_L)^2} + \\ + j \left( X_M + X_s - \frac{(X_A + X_L) X_K^2}{(R_A + R_L)^2 + (X_A + X_L)^2} \right)$$

» By optimal conditions for efficiency and appliance power:

$$Z_s = R_s + \frac{\omega^2 k_I^2 L_A L_s}{R_A + \sqrt{R_A^2 + \omega^2 k_I^2 L_A L_s \frac{R_A}{R_s}}}$$



# Outline

- » Introduction
- » Efficiency
- » Power balance
- » Input impedance
- » Conclusion



# Conclusion

- » The general circuit model for WPT by electromagnetic induction was shown.
- » The efficiency was mentioned.
- » The power balance in the terms of normalized powers was derived.
- » The input impedance was presented.

